
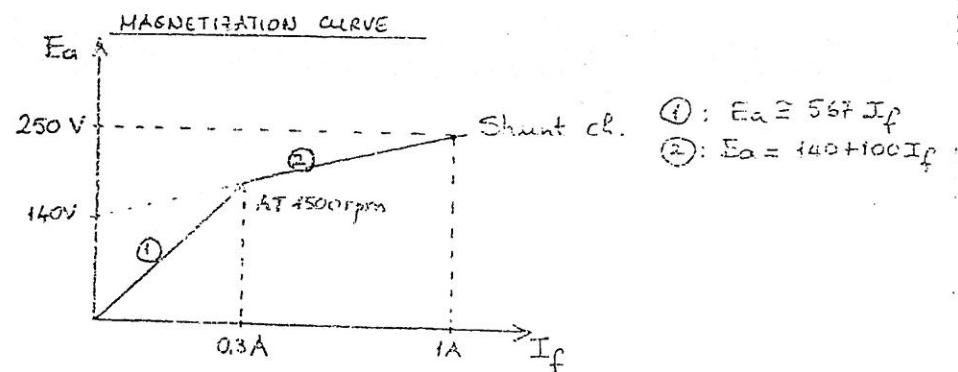


Ex 3

A cumulatively compounded long-shunt connected dc generator delivers 15 A to a  $10 \Omega$  load.

$$r_a + r_s = 1 \Omega \quad r_f = 250 \Omega, \quad \frac{N_f}{N_s} = 52$$

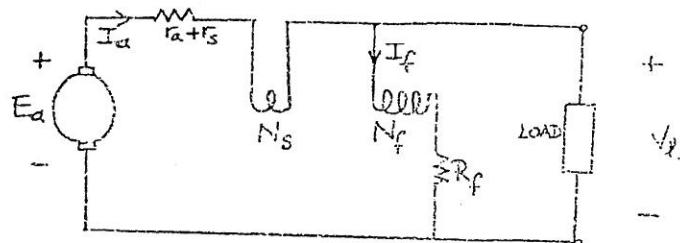The magnetization curve is as shown below. Find the shaft speed in rpm and the electrical torque produced.



Soln

Terminal voltage under load:  $15 \times 10 = 150 \text{ V}$

$$I_f = \frac{150}{250} = 0.6 \text{ A} \Rightarrow I_a = I_f + I_L = 15.6 \text{ A}$$

$$E_a = V_f + I_a(r_a + r_s) = 150 + 15.6 = 165.6 \text{ V}$$

$$\begin{aligned} \text{Total mmf applied} &= \text{Shunt field mmf} + \text{Series field mmf} \\ &= N_f I_f + N_s I_a \end{aligned}$$

$$\begin{aligned} \text{Equivalent shunt field amp: } I_f' &= I_f + \frac{I_a N_s}{N_f} = 0.9 \text{ A} \\ E_a' &= 140 + 100 I_f' = 230 \text{ V at } 1500 \text{ rpm.} \end{aligned}$$

$$\frac{E_a|_{1500}}{E_a|_N} = \frac{1500}{N} \Rightarrow N = \frac{1500 \times 165.6}{230} \approx 1075 \text{ rpm. //}$$

$$\text{Electromagnetic torque} = \frac{E_a I_a}{\omega}$$

$$T = \frac{165.6 \times 15.6 \times 60}{2\pi \times 1075} = 23 \text{ Nm. //}$$

# EE 361 Dec 2005

## Solved Problems

Ex 2

A 200V dc series motor has the following O.C.C. measured at 1000 rpm (O.C.C. is obtained by separately exciting the field winding).


Field Amps, $I_f$	5	10	15	20	25	30
Open-circuit voltage, $E_a$ , Volts	80	160	202	222	236	244

The armature resistance is  $0.25\Omega$  and the series field resistance is  $0.25\Omega$ .

Find the speed of the m/c when,

- the armature current is 22.5 A
- the gross torque is 36 Nm  
( $T_e = T_f + T_{fsw}$ )

Solution

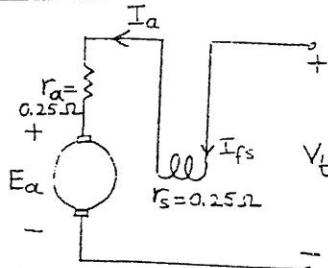

The induced armature emf  $E_a$  at the unknown speed is:  

$$E_a = V_t - I_a(r_a + r_s)$$

$$= 200 - 22.5 \times 0.5 = 188.75 \text{ V}$$

Now, assume that the motor is running at 1000 rpm and supplying the same armature current  $I_a = I_{fs} = 22.5 \text{ A}$ .

From the magnetization curve,

When  $I_{fs} = 22.5 \text{ A}$ ,  $E_a = 230 \text{ V}$

Since  $E_a = K I_a \omega$  &  $I_a$  remains unchanged for both cases,

$$\left| \frac{E_{a,1000}}{E_{a,N}} \right| = \frac{1000}{N} \Rightarrow N = 819 \text{ rpm}$$

$$I_a = 22.5 \text{ A}$$

b) When  $T = 36 \text{ Nm}$ , Find  $N$


For a series motor  $T = K I_a^2$  and when  $T$  is constant,  $I_a$  is also constant & independent of shaft speed.

$$T = \left( \frac{E_a}{\omega} \right) I_a \quad \leftarrow (\text{Ea}/\omega \text{ ratio is constant})$$

Assume the machine is running at 1000 rpm:

$$36 \left( 1000 \times \frac{\pi}{60} \right) = E_a I_a$$

from which  $E_a I_a = 3765$

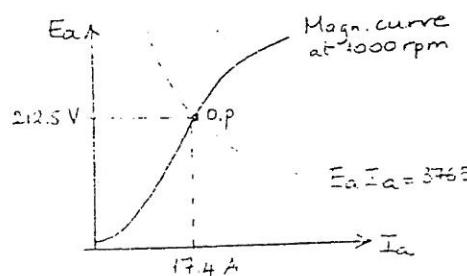

For the unknown speed  $N$ :

$$E_a = V_t - I_a(r_a + r_s)$$

$$= 200 - 17.4 \times 0.5$$

$$= 191.3 \text{ V}$$

↑  
actual value

$$\left| \frac{212.5}{191.3} \right| = \frac{1000}{N} \Rightarrow N = 902 \text{ rpm} //$$

$$I_f = I_a = 17.4 \text{ A}$$

2/13

(A) (B)

Q.4. (22 points) A 15-kW 200-V separately excited dc motor has a field resistance of 200  $\Omega$  and an armature resistance of 0.2  $\Omega$ . The magnetization characteristic of the motor measured at 1500 rpm is given as:

$I_a$ A	0.2	0.4	0.6	0.8	1.0	1.2	1.4	1.6
$E_a$ V	45	90	134	176	210	240	260	270

The speed of the motor is controlled by independently adjusting the armature and field circuits' terminal voltages. For this purpose, both the armature and field circuits are fed with separate variable voltages whose maximum value is 200 V for both circuits.

Armature reaction and rotational losses are to be neglected.

- Calculate the shaft speed and load torque when the motor is supplying 10 kW to its load with maximum voltage applied to both field and armature circuits.
- Now the shaft speed is to be reduced to 1100 rpm while the motor is supplying the same power as in part (a). State how you can achieve this. Assuming that the uncontrolled variable is kept at its maximum value, calculate the new value of the control parameter to satisfy this condition.
- This time the shaft speed is to be increased to 1600 rpm while the motor is supplying the same torque as in part (a). State how you can achieve this. Assuming that the uncontrolled variable is kept at its maximum value, calculate the new value of the control parameter to satisfy this condition.

Solution:

a)  $P_o = 10000 = E_a I_a = P_e$ ,  $V_t = 200V$ ,  $V_f = 200V$   
 $I_f = 200/200 = 1A$ ,  $n$ ,  $T \rightarrow ?$

$$\begin{aligned} E_a &= 10000 \\ E_a &= V_t - R_a I_a = 200 - 0.2 I_a \\ (200 - 0.2 I_a) I_a &= 10000 \end{aligned}$$

$$0.2 I_a^2 - 200 I_a + 10000 = 0 \Rightarrow I_a = 52.8 A$$

$$E_a = 200 - 0.2 \times 52.8 = 189.4 V$$

$$I_f = 1 \rightarrow n = 1500 \rightarrow E_c = 210 V$$

$$I_f = 1 \rightarrow n = ? \rightarrow E_a = 189.4 \quad n = 1500 \frac{189.4}{210} = 1353 \text{ rpm}$$

$$\omega_m = 2\pi \frac{1353}{60} = 141.68 \text{ rad/sec}, T = \frac{P_e}{\omega_m} = \frac{10000}{141.68} = 70.57 \text{ Nm}$$

b)  $n = 1100 \text{ rpm}$ ,  $P_e = 10000 \text{ W}$ . Take  $V_f = 200 \text{ V}$  and  $I_f = 1 A$

$$I_f = 1 \rightarrow n = 1500 \rightarrow E_c = 210 \quad E_a = 210 \frac{1100}{1500} = 154 V$$

$$P_e = E_a I_a, I_a = \frac{10000}{154} = 64.9 A, V_t = E_a + R_a I_a = 154 + 0.2 \times 64.9 = 167 V$$

The speed is reduced by the terminal voltage, keeping flux constant.


c)  $n = 1600 \text{ rpm}$ ,  $T = 70.57 \text{ Nm}$ ;  $P_e = T \cdot \omega_m$ ,  $\omega_m = 2\pi \frac{1600}{60} = 167.55 \text{ rad/sec}$ ,  $P_e = T \cdot \omega_m = 70.57 \times 167.55 = 11824.1 \text{ W}$ . Take  $V_t = 200 \text{ V}$

$$E_a I_a = P_e = (V_t - R_a I_a) I_a \rightarrow 0.2 I_a^2 - 200 I_a + 11824.1 = 0 \rightarrow I_a = 63.1 A$$

$$E_c = 200 - 0.2 \times 63.1 = 187.4 V, \text{ at } n = 1600 \text{ rpm}$$


$$\text{At } n = 1500 \quad E_a = 187.4 \frac{1500}{1600} = 176 V \rightarrow I_f = 0.8 A \rightarrow V_f = 160 V$$

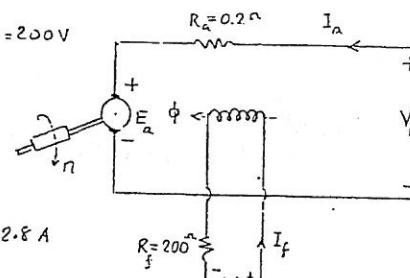The field voltage is increased to 160 V at 1500 rpm to maintain 200 V at 1600 rpm.



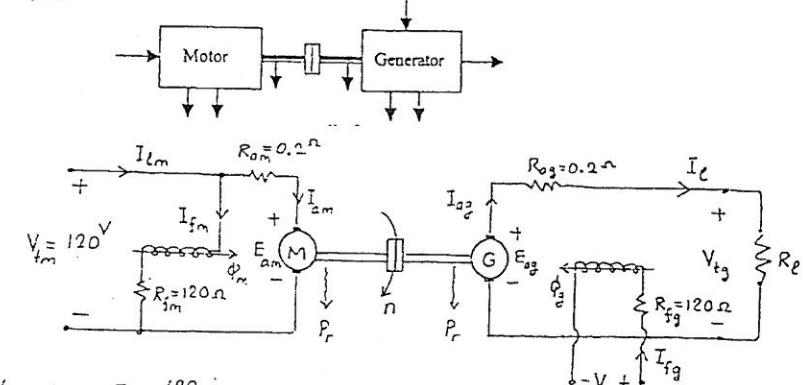Q.4. (22 points) Consider two identical dc machines having an armature resistance  $R_a = 0.2 \Omega$  and a field winding resistance  $R_f = 120 \Omega$ . One of the machines is used as a shunt motor to drive the other to operate it as a separately excited generator to give power to a load. The shunt motor draws 6 kW from a constant voltage source of 120 V. The excitation currents of both machines are equal and the rotational loss of each machine is constant and is 200 W per machine.


- Draw the complete circuit diagram indicating voltages, currents and winding resistances. Use subscript "m" and "g" for motor and generator quantities, respectively.
- Calculate the induced voltage of the motor and of the generator.
- Find the armature current and output power of the generator.
- Complete the power flow diagram of the system given below, by finding the corresponding numerical values for each arrow. Calculate the overall efficiency of the system.



b)  $V_{tm} = 120 V, I_{fm} = \frac{120}{120} = 1 A = I_{fmg}, R_{fa} = R_{fg} = 120 \Omega, V_{tg} = 1 \times 120 = 120 V$   
 $P_{im} = 6000 = V_{tm} \times I_{lm}, I_{lm} = \frac{6000}{120} = 50 A, I_{am} = 49 A$   
 $E_{am} = V_{tm} - R_{am} I_{am} = 120 - 49 \times 0.2 = 110.2 V$   
 $P_{em} = E_{am} I_{am} = 110.2 \times 49 = 5399.8, P_{om} = P_{em} - P_r = 5399.8 - 200 = 5199.8 W$

c)  $E_{eg} = E_{am} = 110.2 V \text{ as } \phi_m = \phi_g = \phi, K_{am} = K_{ag}, \omega_m = \omega_g, E_a = K_a \phi \omega_m$

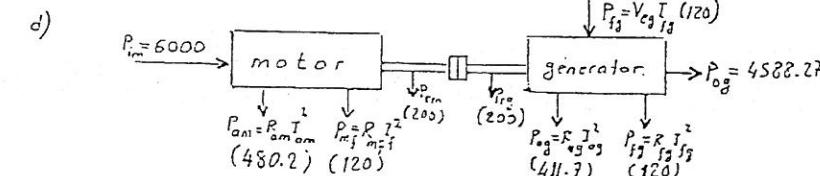c)  $E_{eg} = 110.2 V: P_{om} = P_{ig} = 5199.8 W, P_{eg} = P_{ig} - P_r = 5199.8 - 200 = 4999.8 W$   
 $I_{ag} = \frac{P_{eg}}{E_{eg}} = \frac{4999.8}{110.2} = 45.37 A = I_{cg}, V_{tg} = E_{eg} - R_{ag} I_{cg} = 110.2 - 0.2 \times 45.37 = 101.13 V$   
 $P_{og} = V_{tg} \times I_{cg} = 101.13 \times 45.37 = 4588.27 W$



$$\sum P_{in} = 6000 + 120 = 6120 W, \sum P_{loss} = 480.2 + 120 + 2 \times 200 + 411.7 + 120 = 1531.9 W$$

$$\eta = \frac{\sum P_{out} - P_{loss}}{\sum P_{in}} = \frac{6120 - 1531.9}{6120} = 74.97\%$$

- (A) Q.1. (22 points) Consider the cylindrical relay shown below. The diameter of the plunger is 2 cm and the initial length of the air gap is 4 mm. The exciting coil has 3141 turns.

The relay is excited by a sinusoidal voltage  $v(t) = 310 \cos 100\pi t$  V.

- a) Neglecting coil resistance and leakage flux, calculate the maximum flux density in the air gap.

- b) Comment on the input current shape if the core is infinitely permeable.

- c) What happens to the current waveform if the core has a nonlinear B-H characteristic?

Now, assume that the core material of the relay is infinitely permeable.


- d) Find an expression for the inductance of the core as a function of plunger position  $x$  ( $\mu_0 = 4\pi \cdot 10^{-7}$  H/m).

- e) Find an expression for the instantaneous force acting on the plunger as a function of  $x$  and the current in the coil.

- f) Calculate the initial magnetic force acting on the plunger if the coil current is  $I = 1$  A.

Solution:

$$a) v = 310 \cos 100\pi t$$

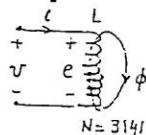


$$v = e = N \frac{d\phi}{dt}$$

$$N = 3141$$

$$\dot{\phi} = \frac{1}{N} \int v dt = \frac{310}{N\omega} \sin \omega t$$

$$\dot{\Phi}_{mx} = \frac{310}{N\omega}, B_{mx} = \frac{\dot{\Phi}_{mx}}{A}, A = \pi r^2 = \pi \times 0.01^2$$
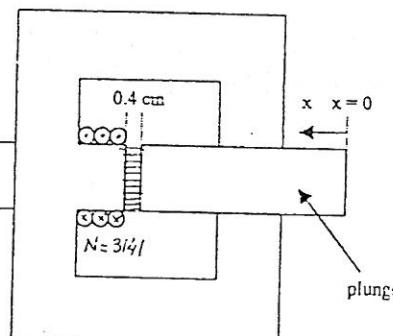
$$B_{mx} = \frac{310}{3141 \times 100\pi \times 0.01^2 \times \pi} \approx 1 \text{ T}$$



- b) If  $\mu \rightarrow \infty$ , the system is linear and the current shape will be the same as input voltage, i.e. sinusoidal.


- c) In case, the core has a non-linear B-H characteristic, the current shape will be distorted if peak flux pushes the core into saturation. Otherwise, the current shape will remain sinusoidal.

$$d) L = N^2/R, R = \frac{g}{\mu_0 A} = \frac{(0.004-x)}{4\pi \cdot 10^{-7} \cdot \pi \cdot 0.01^2} = 25.33 \times 10^8 (0.004-x), L = \frac{N^2}{R} = \frac{3.89 \times 10^8}{(0.004-x)}$$

$$e) F(x) = \frac{1}{2} i^2 \frac{dL}{dx} = \frac{i^2}{2} \frac{3.89 \times 10^8}{(0.004-x)^2}$$

$$f) \text{Let } i = 1 \text{ A}, x_0 = 0, F = \frac{1}{2} \frac{3.89 \times 10^8}{0.004^2} = 121.6 \text{ N}$$

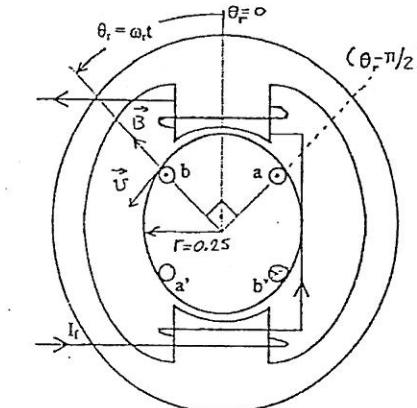- (B) Q.2. (22 points) Consider the simple electric brake shown below. The rotor winding consists of two identical shorted loops, each having a resistance of  $0.005 \Omega$ . The stator winding produces a flux density distribution in the air gap given by  $B(\theta_r) = 1.0 \cos \theta_r$  T. The axial length and diameter of the rotor are both 0.5 m. The core material is infinitely permeable. The rotor is rotating at a speed  $\omega_r = 154 \text{ rad/sec}$ , so that  $\theta_r = \omega_r t$ .



- a) Derive expressions for the emf and for the currents in each of the shorted loops as a function of time. Hint:  $e = I \cdot (\vec{v} \times \vec{B})$

- b) Show that the total power dissipated in the two loops is constant over each revolution, provided that  $\omega_r$  and  $I_r$  are constant.

- c) Given that the field winding self-inductance is  $L_f = 100 \text{ mH}$ , the self-inductance of armature coil a-a' is  $L_a = 0.10 + 0.05 \cos 2\theta_r \text{ mH}$  and the mutual inductance between field and armature coil a-a' is  $M_{fa} = 0.2 \cos \theta_r \text{ mH}$ , find the self and mutual inductances of coil b-b'. Derive an expression for the electromagnetic torque acting on the rotor as a function of time.

Solution:  $L_f = 100 \text{ mH}, L_a = 0.10 + 0.05 \cos 2\theta_r \text{ mH}$

$$M_{fa} = 0.2 \cos \theta_r, B(\theta_r) = 1 \cos \theta_r \text{ T}, l = 0.5 \text{ m}, D_r = 0.5 \text{ m}$$

$$\theta_r = \omega_r t, \omega_r = 154 \text{ rad/sec}, R = 0.005 \Omega = 5 \times 10^{-3} \Omega$$

$$a) v = r\omega_r = 0.25 \times 154 = 38.5 \text{ m/s}$$

$$e_b = 2 \times vLB = 2 \times 38.5 \times 0.5 \times \cos \theta_r = 38.5 \cos \theta_r$$

$$e_a = 2 \times vLB = 2 \times 38.5 \times 0.5 \times \cos(\theta_r - \pi/2) = 38.5 \sin \theta_r$$


$$i_b = \frac{38.5}{R} \cos \theta_r = 7.7 \times 10^3 \cos \theta_r \text{ A}, i_a = 7.7 \times 10^3 \sin \theta_r$$

$$b) \text{Instantaneous power } P(t) = R(i_a^2 + i_b^2) = 5 \times 10^{-3} (7.7 \times 10^3)^2 (\sin^2 \theta_r + \cos^2 \theta_r)$$

$$P = 296450 = \text{constant} \Rightarrow \int_{\theta_r=0}^{\pi} P d\theta_r = P \times 2\pi = \text{constant}.$$

$$c) \text{If } L_a = 0.1 + 0.05 \cos 2\theta_r \text{ mH, } 90^\circ \text{ angle between axes of aa' and bb' coils.}$$
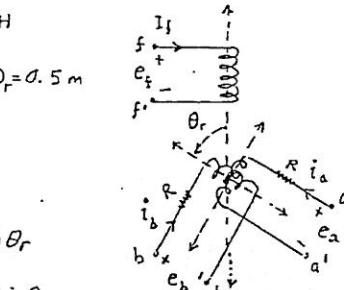
$$L_b = 0.1 + 0.05 \cos 2(\theta_r - 90^\circ) \text{ mH}, M_{fb} = 0.2 \cos(\theta_r + \pi/2) \text{ mH and } M_{ab} = 0 = 0.2 \sin \theta_r$$



Q.3. (35 points) A 2-pole shunt dc generator has an approximate magnetization characteristic measured at 1500 rpm as given below.

$$\begin{aligned} E_a &= 20 \text{ Volts} && \text{if } 0 \leq I_f \leq 0.1 \text{ A} \\ E_a &= 200I_f \text{ Volts} && \text{if } 0.1 \leq I_f \leq 0.5 \text{ A} \\ E_a &= 100I_f + 50 \text{ Volts} && \text{if } 0.5 \text{ A} \leq I_f \end{aligned}$$

where  $I_f$  is the shunt field current.

The armature has a resistance of  $0.2 \Omega$ , and the field circuit has a resistance of  $129.15 \Omega$ .

Throughout the problem the generator is driven at a constant speed of 1500 rpm by its prime mover.

Neglect armature reaction for your calculations.

- Assuming that the machine is operating as a self-excited shunt generator at no-load, sketch the magnetization curve and calculate the armature terminal voltage  $V_t$ .
- The self-excited generator is now loaded by connecting a resistive load to its armature terminals. Calculate the armature terminal voltage  $V_t$  by assuming that the resistive load carries a current of 50 A. Compute also the load resistance.
- The self-excited generator above is now equipped with a series field winding in order to raise the armature terminal voltage in part (b) to 220 V. The series field winding is connected in series with the load so that the machine is converted into a short-compound generator. Calculate the number of series-turns of the series field winding by assuming that the shunt field winding has 1000 turns, and the series field winding resistance is negligibly small. Define also the type of compounding used.
- Compute the efficiency of the self-excited generator in part (b) by assuming that friction and windage losses are 150 W.

### SOLUTION

a)  $R_a = 0.2 \Omega$ ,  $R_t = R_a + R = 129.15 \Omega$

At no-load:  $I_e = 0$ ,  $I_f = \frac{E_a}{R_f}$

$$E_a = (R_a + R_t) I_f = R I_f = V_t \quad ; \quad R = R_a + R_t = 129.35 \Omega$$

$$\begin{matrix} E_a, V_t \\ (V) \end{matrix}$$

250

220




200

150

100

50

20

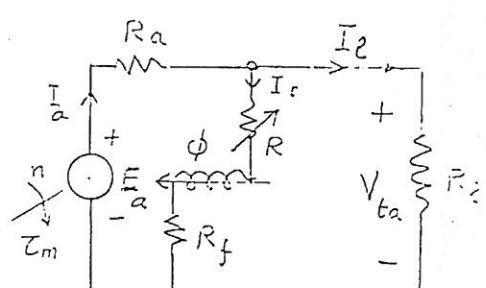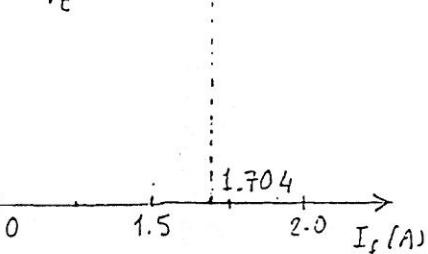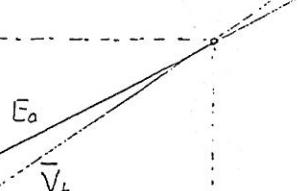

$$V_t = E_a$$

$$129.35 I_f = 50 + 100 I_f$$

$$29.35 I_f = 50$$

$$I_f = 1.706 \text{ A}$$

$$V_{ta} = R_t I_f = 129.15 \times 1.706 = 220$$

Q.3. (35 points) A 2-pole shunt dc generator has an approximate magnetization characteristic measured at 1500 rpm as given below.

$$\begin{aligned} E_a &= 20 \text{ Volts} && \text{if } 0 \leq I_f \leq 0.1 \text{ A} \\ E_a &= 200I_f \text{ Volts} && \text{if } 0.1 \leq I_f \leq 0.5 \text{ A} \\ E_a &= 100I_f + 50 \text{ Volts} && \text{if } 0.5 \text{ A} \leq I_f \end{aligned}$$

where  $I_f$  is the shunt field current.

The armature has a resistance of  $0.2 \Omega$ , and the field circuit has a resistance of  $129.15 \Omega$ .

Throughout the problem the generator is driven at a constant speed of 1500 rpm by its prime mover.

Neglect armature reaction for your calculations.

- Assuming that the machine is operating as a self-excited shunt generator at no-load, sketch the magnetization curve and calculate the armature terminal voltage  $V_t$ .
- The self-excited generator is now loaded by connecting a resistive load to its armature terminals. Calculate the armature terminal voltage  $V_t$  by assuming that the resistive load carries a current of 50 A. Compute also the load resistance.
- The self-excited generator above is now equipped with a series field winding in order to raise the armature terminal voltage in part (b) to 220 V. The series field winding is connected in series with the load so that the machine is converted into a short-compound generator. Calculate the number of series-turns of the series field winding by assuming that the shunt field winding has 1000 turns, and the series field winding resistance is negligibly small. Define also the type of compounding used.
- Compute the efficiency of the self-excited generator in part (b) by assuming that friction and windage losses are 150 W.



### SOLUTION

a)  $R_a = 0.2 \Omega$ ,  $R_t = R_f + R = 129.15 \Omega$

At no-load:  $I_t = 0$ ,  $I_f = \frac{E_a}{R}$

$$E_a = (R_a + R_t) I_f = R I_f = V_t \quad ; \quad R = R_a + R_t = 129.35 \Omega$$
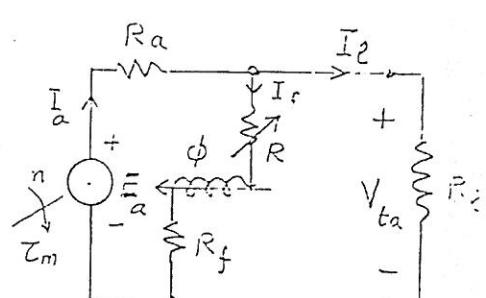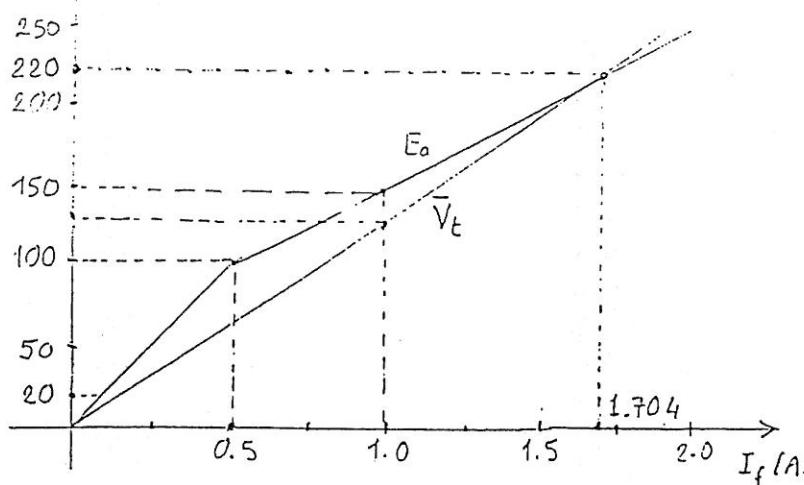
$$\begin{matrix} E_a, V_t \\ (V) \end{matrix}$$



$$V_t = E_a$$

$$129.35 I_f = 50 + 100 I_f$$

$$29.35 I_f = 50$$

$$I_f = 1.706 \text{ A}$$

$$V_{ta} = R_t I_f = 129.15 \times 1.706 = 220$$

b)

$$\begin{cases} I_a = I_\ell + I_f = 50 + I_f \Rightarrow I_\ell = 50 \text{ A} \\ V_{ta} = R_t I_f = 129.15 I_f \\ V_{ta} = E_a - R_a I_a = (50 + 100 I_f) - 0.2 I_a = 50 + 100 I_f - 0.2 (50 + I_f) = 99.8 I_f + 40 \end{cases}$$

$$129.15 I_f = 99.8 I_f + 40 \rightarrow I_f = \frac{40}{29.35} = 1.363 \text{ A} \Rightarrow I_a = 51.363 \text{ A}$$

$$V_{ta} = I_f * R_t = 176 \text{ V}, R_\ell = \frac{V_{ta}}{I_\ell} = 3.52 \Omega$$

c)  $N_f = 1000 \text{ turn}, R_s \approx 0, V_{ta} = 220 \text{ V}$

Assume:  $\phi = \phi_f + \phi_s$

$$R_\ell = 3.52 \Omega, I_\ell = \frac{220}{3.52} = 62.5 \text{ A}$$

$$\bar{I}_f = \frac{220}{129.15} = 1.703 \text{ A}$$

$$I_a = I_\ell + \bar{I}_f = 64.23 \text{ A}$$

$$E_s = V_{ta} + R_a I_a = 220 + 0.2 * 64.2 = 220 + 12.84 = 232.84 \text{ V}$$

The required total equivalent shunt current  $\bar{I}_f$

$$232.84 = 100 \bar{I}_f + 50, \bar{I}_f = \frac{232.84 - 50}{100} \approx 1.83 \text{ A}$$

The corresponding required total shunt mmf is

$$14 \bar{I}_f = 1000 + 1.83 = 1830 \text{ At}$$

The shunt field provides  $1000 * 1.703 = 1703 \text{ At}$

The difference  $E_F = 1830 - 1703 = 127 \text{ At}$  should additionally be provided by the series field winding.


$$N_s I_\ell = 127, N_s \approx \frac{127}{62.5} = 2 \text{ turns}$$

d)  $P_{out} = V_{ta} * I_\ell = 176 * 50 = 8800 \text{ W}$

$$P_f = 129.15 * 1.363^2 = 239.9 \text{ W}, P_a = 0.2 * 51.363 = 527.63 \text{ W}$$

$$P_{in} = P_{out} + P_f + P_r + P_{fw} = 8800 + 239.9 + 527.63 + 150 = 9717.53 \text{ W}$$
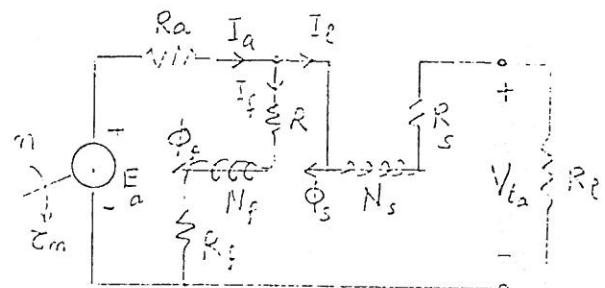
$$\text{Efficiency} = \frac{8800}{9717.53} = 90.6\%$$



Q.4. (60 points) A 200-V 2-pole separately excited dc motor drives a load with a constant torque demand of 191 Nm. The field winding has  $N_f = 1000$  turns.

The magnetization characteristic of the machine is obtained at 1000 rpm, and is approximated by a straight line,  $E_a = 200I_f$  Volts.

Armature resistance  $R_a$  is  $0.2 \Omega$ , friction and windage torque is negligibly small, and the field excitation is kept constant at  $I_f = 1$  A throughout the problem.

(a) Show that the shaft speed versus torque characteristic of the separately excited dc motor operating at steady-state is given by:  $\omega = \frac{V_t}{K_a \phi} - \frac{R_a}{(K_a \phi)^2} T$ ,

where  $\omega$  is the angular shaft speed,  $V_t$  is the applied motor voltage,  $\phi$  is the field flux per pole,  $K_a$  is the motor constant, and  $T$  is the torque.

(b) Calculate the no-load shaft-speed in rpm for  $V_t = 200$  V.

(c) With the same terminal voltage, if, now, the constant-torque load of 191 Nm is applied to the shaft, what will the new shaft speed be? Neglect armature reaction. Comment on the result.

(d) If the speed is to be reduced to 450 rpm by armature voltage control, what should the new value of the applied motor voltage be? Briefly compare speed control techniques by varying the armature voltage and field current.

(e) Suppose now that the speed is to be increased to the no-load value found in part (b) while the machine is operating as in part (c) ( $V_t = 200$  V,  $T_L = 191$  Nm), by equipping the motor with a series field winding of negligible resistance. Determine the type of compounding and the number of turns of the series field winding to be inserted.

(f) Find the shaft-speed for the operating condition in part (c) ( $V_t = 200$  V,  $T_L = 191$  Nm) by assuming that the demagnetizing effect of the armature reaction is  $AR = 2I_a$  Ampere-turns. Briefly discuss the effect of armature reaction on the induced armature emf.

(g) Assume now that the applied motor voltage is suddenly reduced to 100 V, while the motor is operating as in part (c) ( $T_L = 191$  Nm) with armature reaction neglected. Determine the directions and magnitudes of armature current, electromechanical torque and electromechanical power just after this operation by assuming that the speed remains momentarily constant. Also identify the mode of operation of the machine in this case.

8/13

### SOLUTION

$$R_a = 0.2 \Omega, I_f = 1 \text{ A} = \text{const}, E_a = 200I_f \text{ at } n=1000, I_f \downarrow V_f - R_f \parallel V_t = 200 \text{ V}$$

a)  $V_{ta} = R_a I_a + E_a$   
 $E_a = K_a \phi \omega$   
 $T = K_a \phi I_a \rightarrow I_a = \frac{T}{K_a \phi}$

$$V_{ta} = R_a \frac{T}{K_a \phi} + K_a \phi \omega \rightarrow V_{ta} - R_a \frac{T}{K_a \phi} = K_a \phi \omega \rightarrow \omega = \frac{V_{ta}}{K_a \phi} - R_a \frac{V_{ta}}{(K_a \phi)^2}$$

b) For  $I_f = 1 \text{ A}$ ,  $n = 1000 \text{ rpm} \rightarrow E_a = 200 \times 1 = 200 \text{ V} = V_{ta}$  at no-load  
 Thus;  $n = 1000 \text{ rpm}$

c) At  $n_0 = 1000 \text{ rpm} \Rightarrow \omega_0 = 2\pi \frac{1000}{60} = 104.72 \text{ rad/s}$  and  $I_f = 1 \text{ A}$ ,  $\phi_f = N_f I_f = 1000$   
 $E_a = 200 \times 1 = K_a \phi_f \omega_0$ ,  $K_a \phi_f = \frac{200}{104.72} = 1.91$ ,  $T = K_a \phi_f I_a = 191 \text{ Nm}$

$$T = \frac{191}{1000} = 191 \text{ Nm} \cdot 100 \text{ A} \cdot E_a = K_a \phi_f \omega_0 \cdot V_{ta} = E_a + R_a I_a \cdot F = 200 - 0.2 \times 100 = 180 \text{ V}$$

$$I_f = 1 A = \text{const} , E_a = 200 V \quad \text{at } n = 1000 \text{ rpm} \\ " \quad E_a = 180 V \quad \text{at } n = ? \quad \left. \right\} n = 1000 \frac{180}{200} = 900 \text{ rpm}$$

$$\text{Speed regulation} = \frac{1000 - 900}{900} = 11.1\% . \text{ satisfactory.}$$

$$d) I_f = 1 A , n = 1000 \text{ rpm} \rightarrow E_a = 200 V \\ I_f = 1 A , n = 450 \text{ rpm} \rightarrow E_a = ? \quad \left. \right\} E_a = \frac{450}{1000} * 1000 = 90 V$$

$$T = 191 \text{ Nm} \rightarrow I_a = 100 A (\text{part c}), V_{ta} = E_a + R_a I_a = 90 + 0.2 * 100 = 110 V$$

$$e) n = n_o = 1000 \text{ rpm}, V_{ta} = 200 V,$$


$$I_a = 100 A, T = 191 \text{ Nm}, I_f = 1 A$$

$$E_a = V_{ta} - R_a I_a = 200 - 0.2 * 100 = 180 V$$

$$E_a = K_a \phi' \omega, \phi' = \phi_f + \phi_s$$

$$(K_a \phi') = \frac{120}{104.72} = 1.1719$$
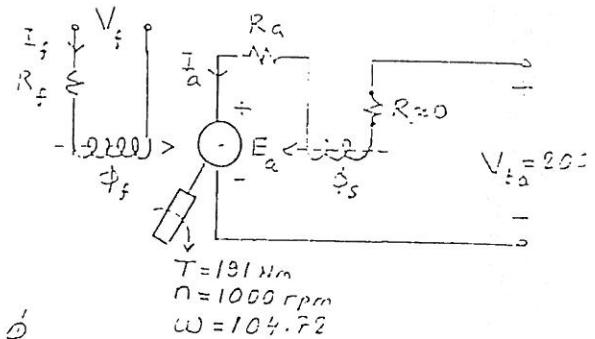
$$\delta(K_a \phi) = 1.91 - 1.1719 = -0.191 \rightarrow \phi = \phi_f - \phi_s$$



(subtractive). Reduction in the generated voltage =  $\delta E_a = 200 - 180 = 20$

$$\text{at } n = 1000 \text{ rpm} \quad I_f = 1, N_f I_f = 1000 \text{ At} \rightarrow E_a = 200 V$$

$$" \quad \delta E_a = 20 V \quad \left. \right\} \delta E_a = \frac{20}{200} * 1000 = 100$$

$$\delta E_a = N_f I_f = N_s I_a = 100 \text{ At}, N_s = \frac{100}{100} = 1 \text{ turn}$$

$$f) V_{ta} = 200 V, I_a = 100 A, T = 191 \text{ Nm}, I_f = 1 A, E_a = 180 V$$

$$n = ?, K_a \phi = ?, E_a = ?$$

$$T = K_a \phi I_a = K F I_a, E_a = K_a \phi \omega = K F \omega, F \rightarrow \text{mmf}$$

$$\text{For } I_f = 1, N_f = 1000, F = 1000, T = 191 = K * 10^3 * 10^2, K = 191 * 10^{-5}$$

$$\text{mmf including armature reaction} = N_f I_f - 2 I_a = 10^3 - 2 I_a$$

$$191 = 191 * 10^{-5} (10^3 - 2 I_a) I_a \rightarrow 1 = 10^{-5} (10^3 - 2 I_a) I_a \rightarrow$$

$$2 I_a^2 - 10^3 I_a + 10^5 = 0 \quad I_a = \frac{10^3 \mp (10^6 - 8 \times 10^5)^{1/2}}{4} = \frac{10^3 \mp 447.2}{4} \Rightarrow I_a = 138.2 A \Rightarrow I_a = 361.8 A$$

$$I_a = 138.2 A, E_a = V_{ta} - R_a I_a = 200 - 138.2 * 0.2 = 172.36 V$$

$$F = (10^3 - 2 * I_a) = (10^3 - 2 * 138.2) = 723.6$$

$$\omega = \frac{E_a}{K F} = \frac{172.36}{191 * 10^5 * 723.6} = 124.71 \rightarrow n = \frac{60 \omega}{2\pi} = \frac{60 * 124.71}{2 * \pi} = 1191 \text{ rpm}$$


$$g) n = 1000 \text{ rpm}, E_a = 180 V, K_a \phi = \text{const} = 1.91$$

$V_t = 100 V < E_a$ ,  $I_a$  and  $T$  changes direction

$$E_a = V_t + R_a I_a, I_a = (180 - 100) / 0.2 = 400 A, P_{out} = 100 * 400 = 40 \text{ kW}$$

$T = K_a \phi I_a = 1.91 * 400 = 764 \text{ Nm}$  re-generative braking (recuperation (generator operation)).

### Ex. Self-excited shunt dc generator

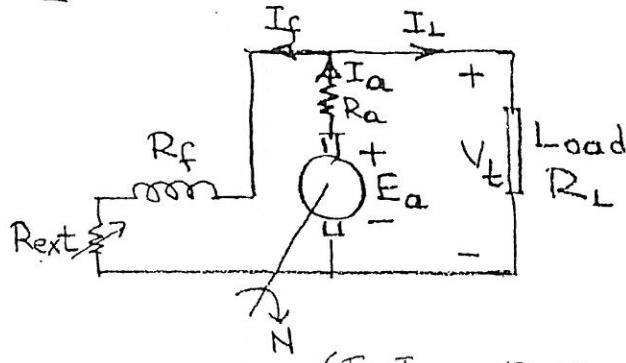

Assumptions:  $R_a, R_f, R_{ext}$  known

$I_L, E_a$  vs  $I_f$  ch. given

Find  $E_a, I_f$  and  $V_t$

At no-load:  $I_L = 0$  and hence

$$(E_a I_a = (R_f + R_{ext}) I_f) \Rightarrow I_a = I_f \quad \text{Net output power} = V_t I_L = 0$$

$$\Rightarrow I_a = I_f$$

$$V_t = E_a - R_a I_a$$

$$= E_a - R_a I_f$$


$$V_t = (R_f + R_{ext}) I_f$$

$$= R'_f I_f$$

$$R'_f I_f = E_a - R_a I_f$$

$$\Rightarrow E_a = (R_a + R'_f) I_f$$

$$E_a \text{ vs } I_f \text{ given}$$

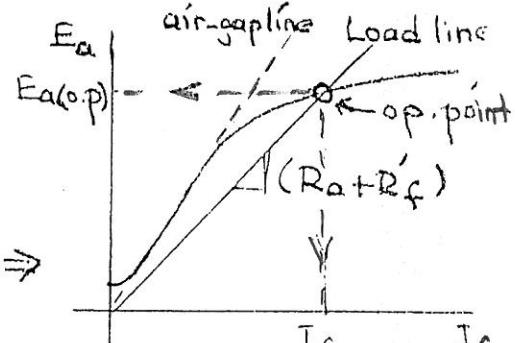


Intersection point between these two chs is the operation point in the S.S

Underload:  $I_L > 0 \Rightarrow V_t I_L > 0, I_a = I_L + I_f$

$$V_t = E_a - R_a(I_f + I_L)$$

$$V_t = I_f R'_f$$
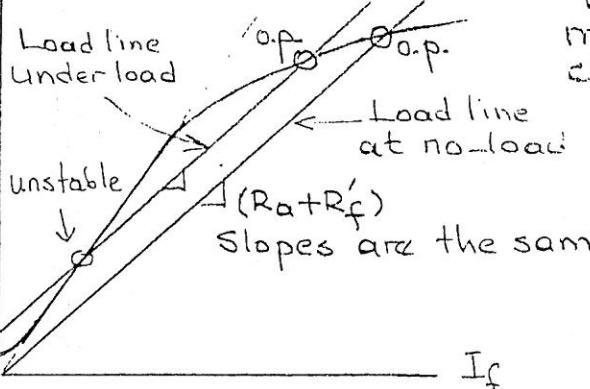
$$\Rightarrow I_f(R_a + R'_f) = E_a - R_a I_L \quad \text{Plot it on the given magnetisation characteristic}$$



Therefore,

$$V_t = E_a - I_a R_a$$

Comment on the result:  
Load connected to the armature terminals causes a drop in terminal voltage.

$$I_L R_a \uparrow$$

$$I_f$$

Ex. If  $R_L$  is known instead of  $I_L$ , compute  $E_a, I_f$  and  $V_t$ .

$$V_t = E_a - R_a I_a$$

$$= E_a - R_a(I_f + I_L)$$

Since  $I_f = V_t / R'_f$  and  $I_L = V_t / R_L$

$$\text{then } V_t = E_a - R_a \left( \frac{V_t}{R'_f} + \frac{V_t}{R_L} \right)$$


$$\text{by rearranging } V_t = E_a \left[ \frac{R'_f R_L}{(R'_f R_L + R_a R_L + R_a R_a)} \right] \dots \textcircled{1}$$

Replace  $V_t$  in Eqn① by  $V_t = R'_f I_f$


This substitution yields:

$$E_a = \left[ R'_f + R_a + \frac{R'_f R_a}{R_L} \right] I_f \dots \textcircled{2}$$

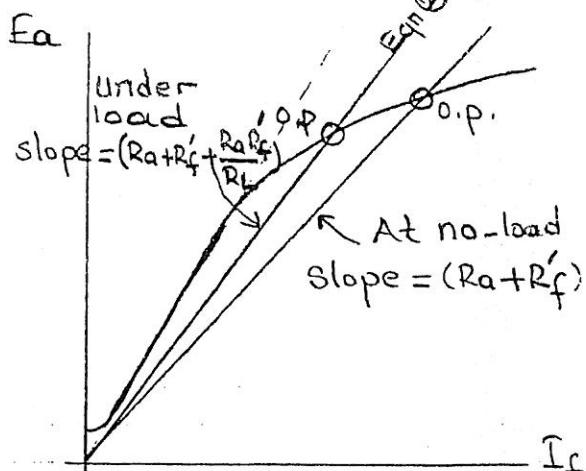
Find the intersection point between  $E_a$  vs  $I_f$  and Eqn②.



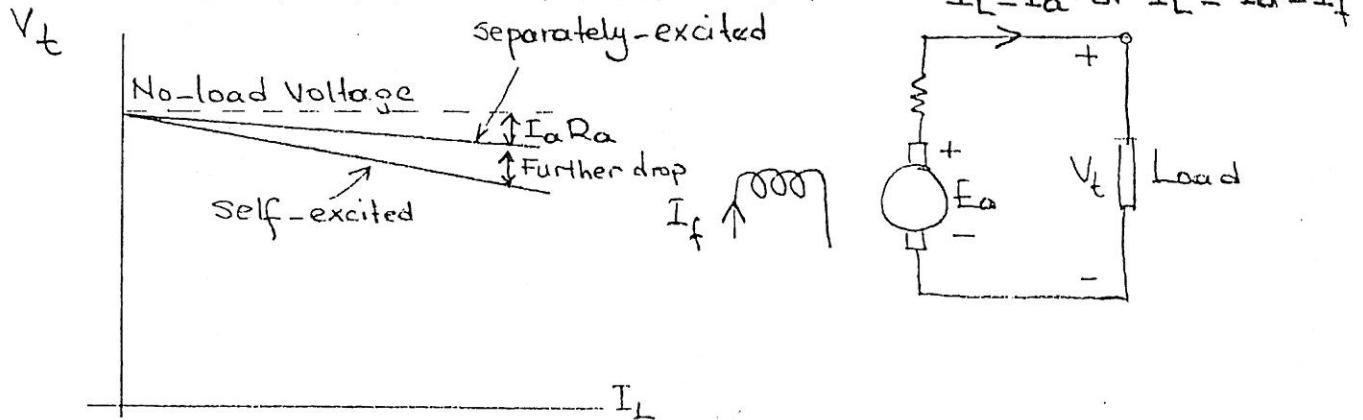
## A Comparison of dc generator terminal characteristics



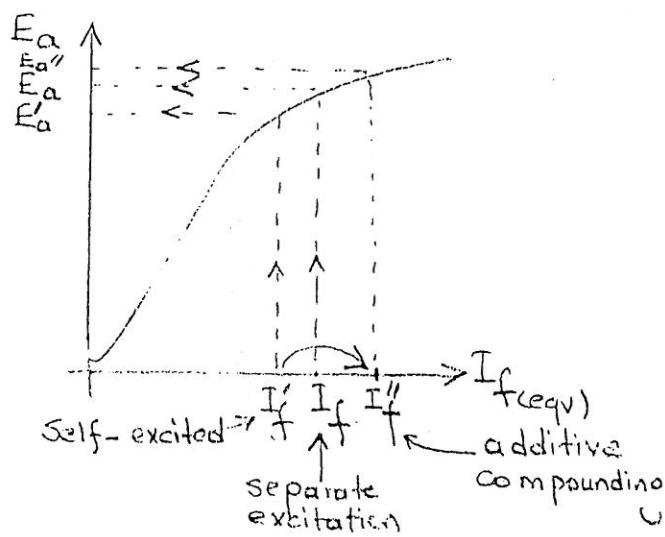For a self-excited dc generator as  $I_L$  is increased  $V_t$  falls further because as  $V_t$  decreases  $I_f = V_t/R_f$  and hence  $E_a$  decrease



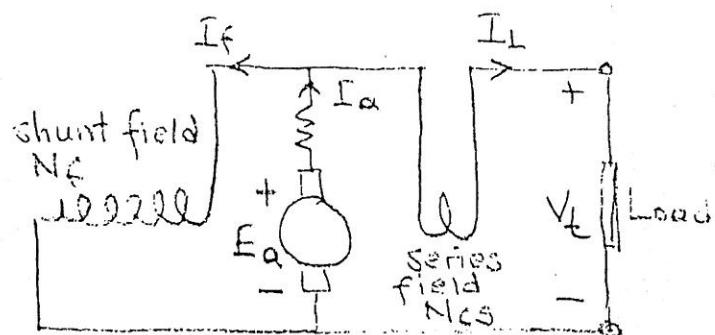To compensate for the fall in terminal voltage as load is increased, additive (cumulative) compounding can be used.



$$\text{Separate excitation: } V_t = E_a - I_a R_a$$

$$\text{Self-excitation: } V'_t = E'_a - I_a R_a$$


$$\text{Gross MMF} \approx N_f I_f + N_{fs} I_a \quad (I_L \approx I_a)$$

$$\text{Equivalent shunt, } I_{f(\text{equiv})} \approx I_f + \frac{N_{fs}}{N_f} I_a$$

$$\text{Cumulative comp: } V''_t = E''_a - I_a R_a$$

11/13

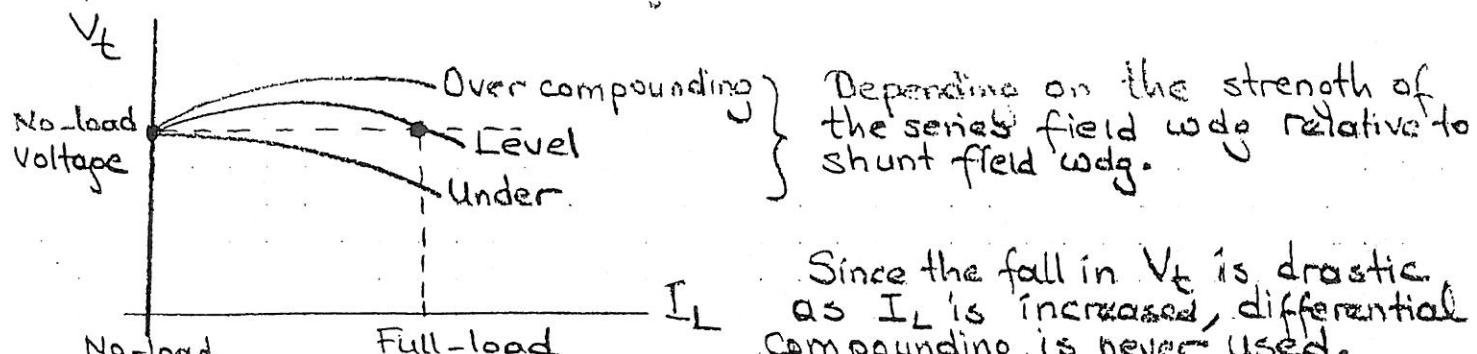
By using cumulative compounding the terminal characteristic of a self-excited generator can be approximated to that of an ideal direct voltage source.




Since the fall in  $V_t$  is drastic as  $I_L$  is increased, differential compounding is never used.

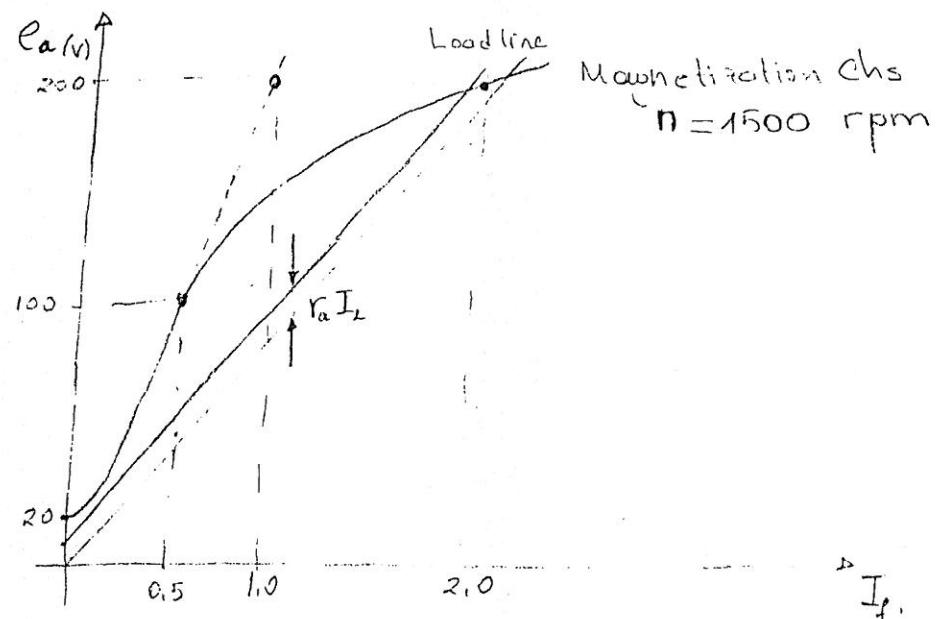Example

A shunt generator has a magnetization characteristic, at  $n=1500$ , as shown in the figure below. The armature has a resistance of  $0.2\Omega$ , and the field has a total resistance of  $100\Omega$ . a) Find the terminal voltage and the field current of the generator, when it delivers  $50\text{ A}$  to a resistive load. b) Find the terminal voltage and the field current when the load is disconnected.



Solution

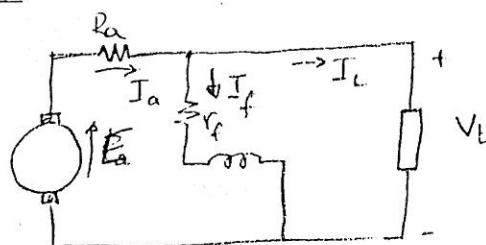

$$\text{Terminal voltage eqn. } E_a - r_a I_a = V_t \quad (1)$$

$$\text{AC so } r_f I_f = V_t \quad (2)$$

$$I_a = I_f + I_L \quad (3)$$

From eqns. (1), (2) and (3)

$$E_a = r_a (I_f + I_L) + r_f I_f$$

$$E_a = (r_a + r_f) I_f + r_a I_L$$

$$= 100.2 I_f + 10 \quad (4)$$

12/13

$E_a$ (q) is the load line. Solutions for  $E_a$  and  $I_f$  are at the intersection point of the magnetization characteristic with the load line.

$$E_a \approx 200 \text{ V} \quad I_f \approx 1.9 \text{ A}$$

$$I_a = 51.9 \text{ A} \Rightarrow V_t = 200 - (0.2) \times 51.9 \approx 190 \text{ V.}$$

b) When the load is disconnected, the load line becomes

$$E_a = 100.2 I_f \quad (E_a = (R_a + R_f) I_f)$$

$$\Rightarrow I_f \approx 2.1 \text{ A} \Rightarrow V_t = 210 \text{ V}$$

$$V_t = E_a - I_f R_a \approx 210 \text{ V}$$

The effect of commutator reaction is due to the reduction in the field flux  $\Phi_d$ . Since  $E_a = K_d \Phi_d W$ , a reduced flux will cause the induced armature emf  $E_a$  to decrease. The effect of armature reaction then is approximately the same as a demagnetizing mmf  $AR$  acting on the main field axis or a d-axis.

The net direct-axis mmf is then assumed to be

$$\text{Net mmf} = \text{Gross mmf} - AR$$

$$= N_f I_f + N_s I_s - AR$$

Example: A 200 V, 3.5 kW dc motor drives a millimeter load, at 1500 RPM. At this speed, the no-load voltage is 275 Volts and armature current = 15 Amps.

Developing armature reaction must act on d-axis i.e.


$$\text{given } AR = 4 \times I_a \text{ AT}$$

1000 turn field coil has a resistance of 200 Ohms.

You are given the magnetization curve ( $E_a$  vs.  $A$ ) of the mc.

Find  $E_a$  and net output power in hp.

Solution:

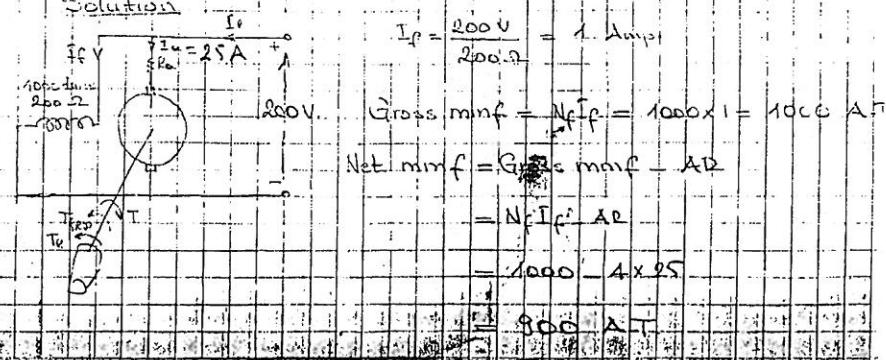

From the magnetization curve

When Net mmf = 900 AT,  $E_a = 190 \text{ Volts}$

Gross output power =  $E_a I_a = 190 \times 2.1$

= 1750 Watts (Energy converted to mechanical form)

Net output power = 1750 - Mechanical rotational losses = 1750 - 275

= 1475 Watts =  $\frac{1475}{746} = 6 \text{ H.P.}$

13/13